

# MULTI- MEGA- PHONE



Agente Costura  
WITH  
Federica Teti!

## MATERIAL:

- 3 potentiometers 100Kohm
- 3 widerstand 100kohm
- 1 kondensator 10uF
- 1 kondensator 220uF
- 1 IC LM 386
- 1 IC halter
- 1 Lautsprecher
- 3 Klinken-Buchse (6,35mm)
- 1 Kippschalter
- 1 batterie clip


1 lochrasterplatine

0,14mm Litze verschiedene  
Farben

MIKRO:




- piezo
- Mikrofonkabel
- klinken-Stecker (6,35mm)

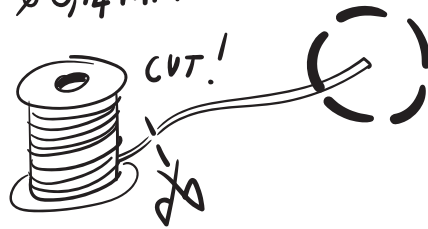LITZE (KABEL)  
shielded wire  
(lead)  
Ø 0,14 mm




Cut 3 leads of each color of  
about 10cm (depending on the  
housing).


Remove shield at  
the tip and TWIST!

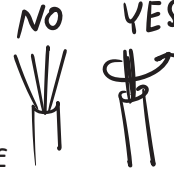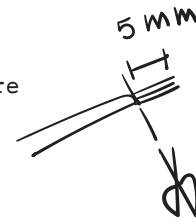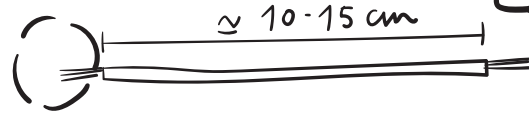

RESPECT  
COLOR CODING!

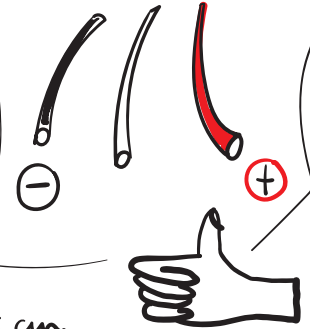


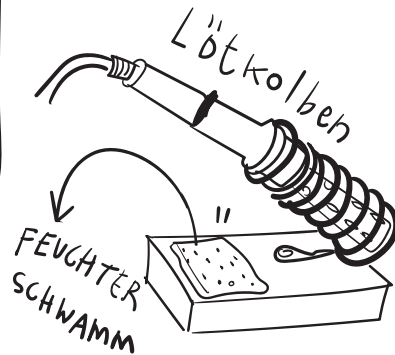It will make life easier  
for troubleshooting!



TINNING!

LÖTEN!

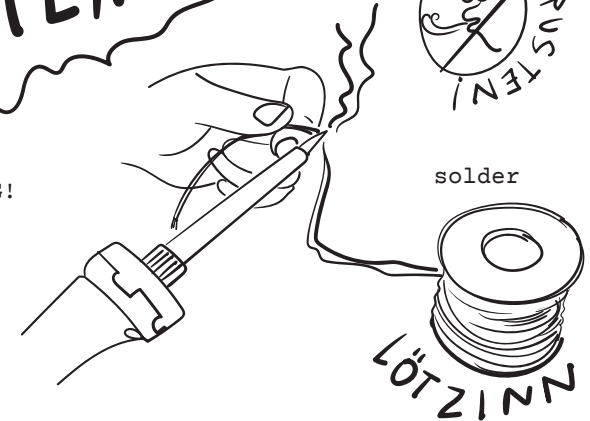


Apply heat to the metal (a few  
seconds) then apply solder.  
Tinning means coating the leads  
and connection points before  
soldering them together:  
this makes stronger connections!









A potentiometer is a three-terminal resistor with a sliding or rotating contact that forms an adjustable voltage divider.

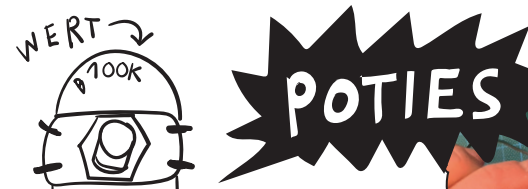Tin the poties then join the leads to each terminal following the color code.



# POTIES

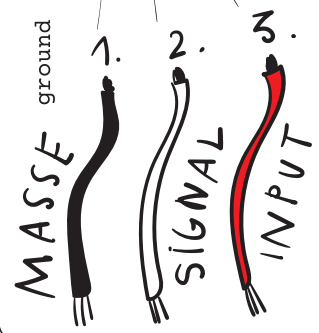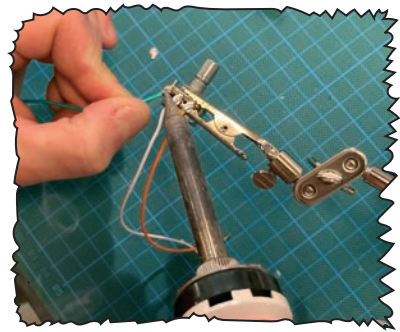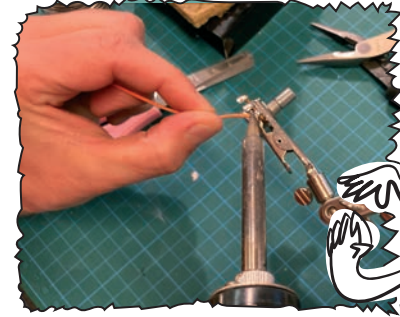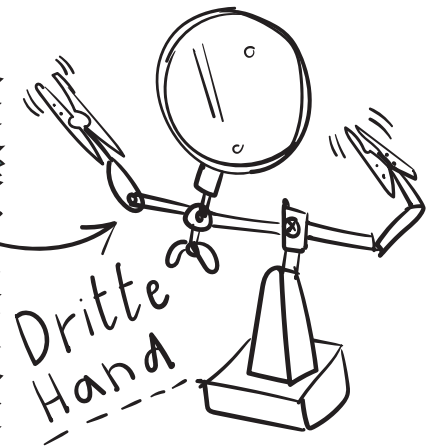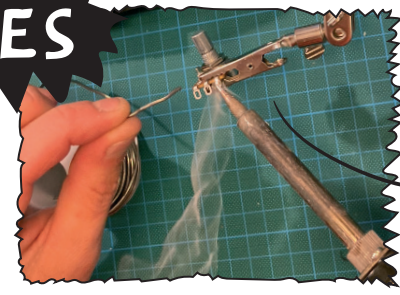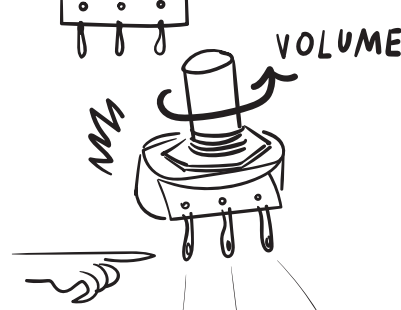

resistor


# WIDERSTAND

100kΩ = WIE DIE POTIES


KEINE POLARITÄT



BIEGEN

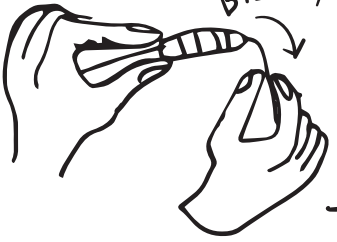

Rein STECKEN

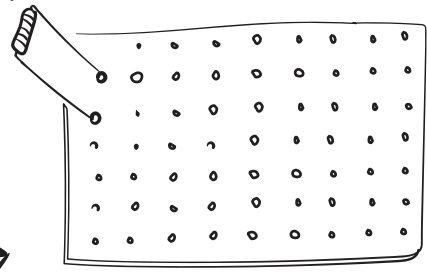

# PLATINE

circuit board





A resistor is a passive electrical component that limits electrical current to a specific value.


The circuit board we are using has single copper holes, we have to make all the connections.

Always place components on the top (plastic) and solder on the bottom (copper)!

PLATINE

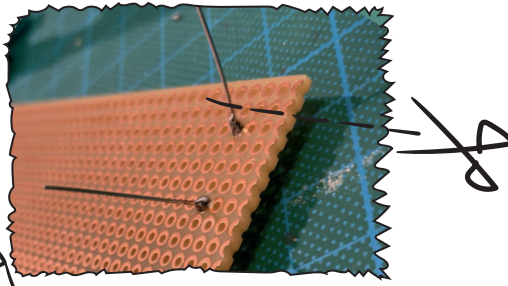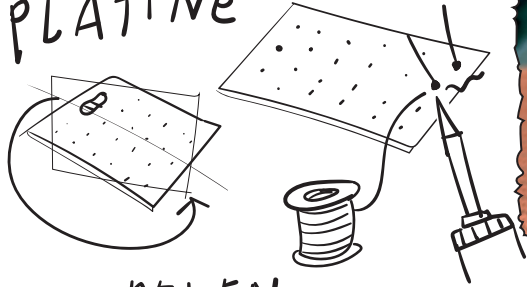

UMDREHEN & LÖTEN!

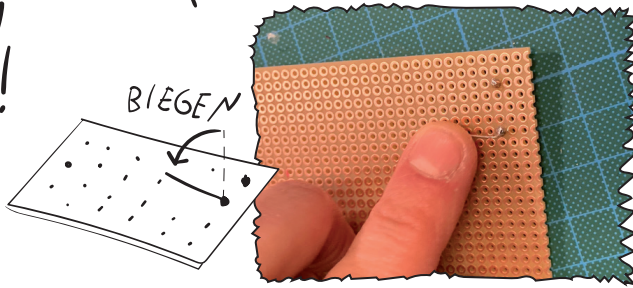

Turn the board and solder.  
Heat the metal first then apply solder.  
Solder joints should look like small shiny blobs.  
Cut the top leg and keep it for later.  
Bend the bottom leg, it will be a bridge between resistors.



Channel 1:

1 Thread the lead into the hole until the shield and solder in place.

Join white lead from the poti with the top resistor leg by soldering the two joints together.



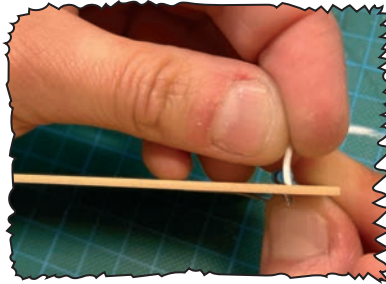
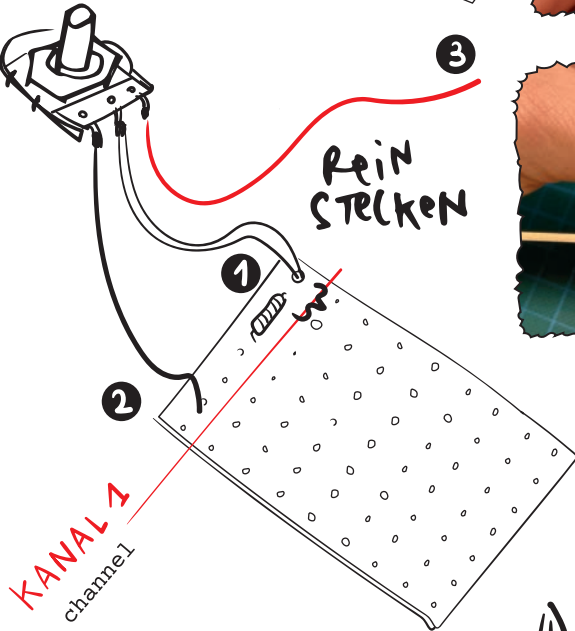
2 Solder the ground (black) lead a few holes down on the board. This is the beginning of a ground path!




3 The socket is the connector for the microphone (input).  
Check the socket polarity (see -->Mikro) and connect + to poti and - to ground!

! POLARITÄT ACHTEN WO + & -




Tin first then join!

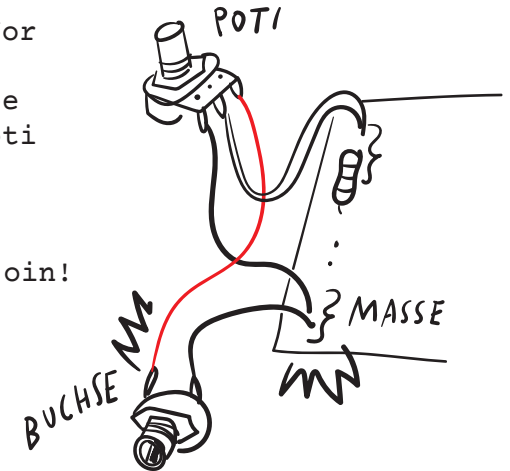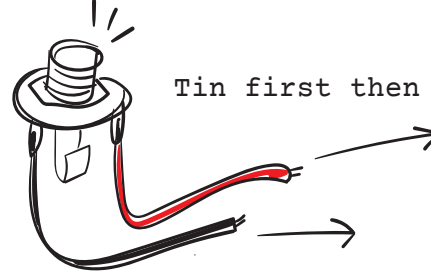

BUCHSE: INPUT

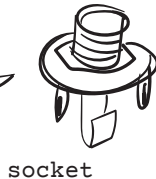


socket

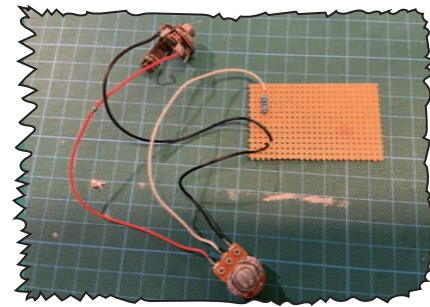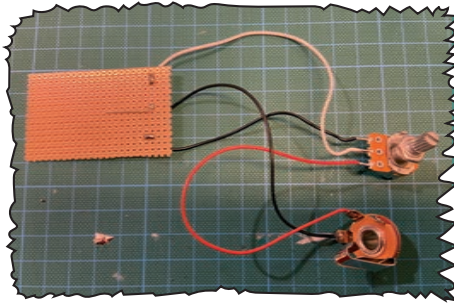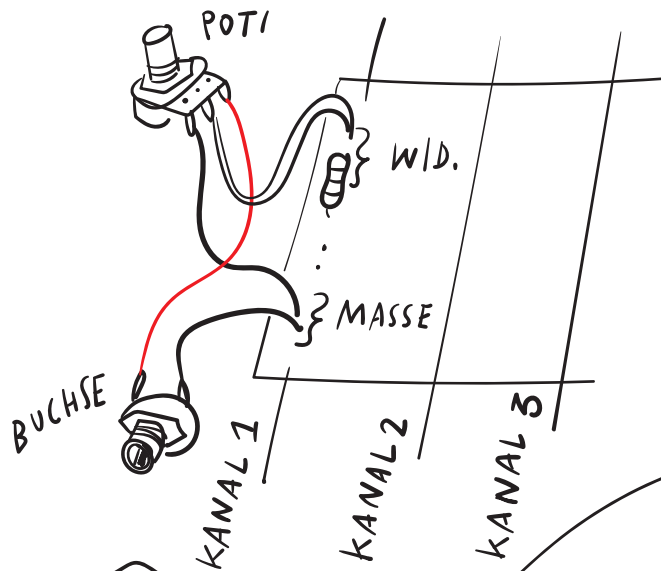


Do the same for channel 2 and 3!

Connect the bent legs of the three resistors.

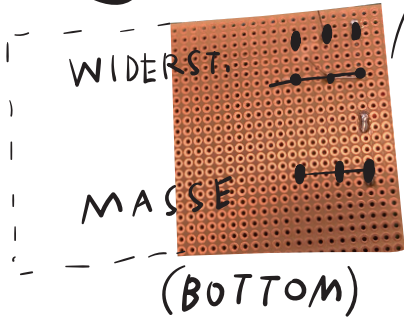Use the cut out resistors legs to connect all ground joints.



IT SHOULD LOOK LIKE THIS!

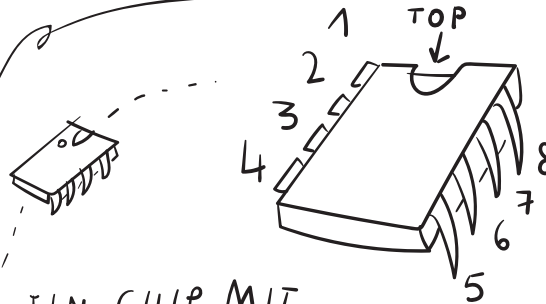

EIN CHIP MIT 8 PINS (BEINCHEN)

The LM386 is an operational amplifier! Each pin has a specific function in the circuit.




If the chip is placed upsidewind it may burn...
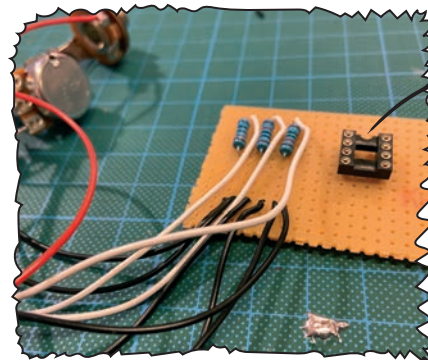
# INTEGRATED CIRCUITS




An integrated circuit is a set of electronic circuits on one small flat piece (or "chip") of semiconductor material. ICs have revolutionized electronics!




This is an IC holder. It also has a marker at the top! Place it on the board so pin 3 is aligned with resistors.

# CONNECTIONS

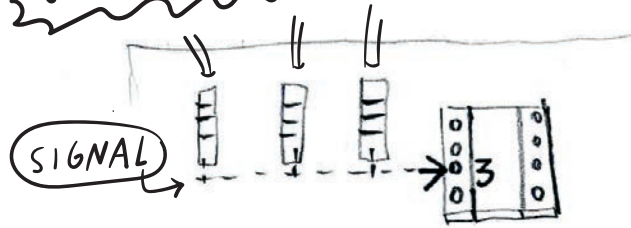

Solder each pin to board and make sure they do not connect to each other. From now on all joints will be very close to each other. Be precise!

Connect the row of resistors to pin 3.

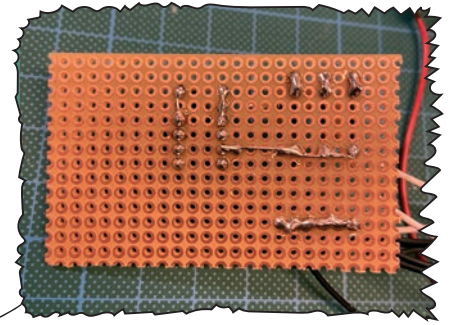


# 10µF KONDENSATOR capacitor

POLARITÄT

KURZES BEIN

Rein STECKEN

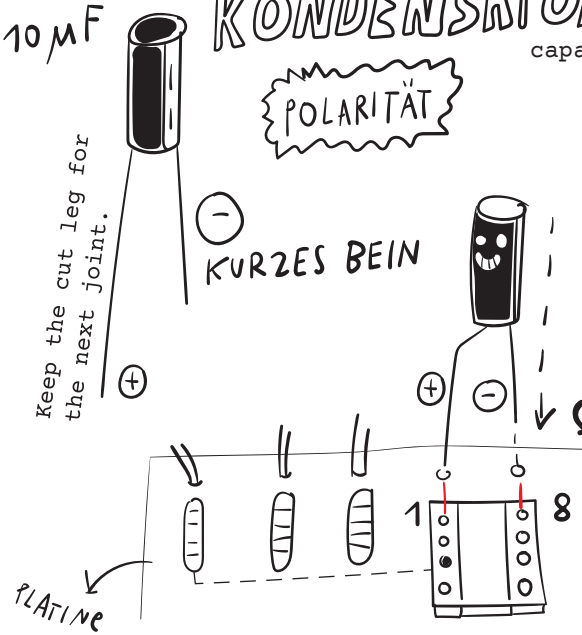



Electrolytic capacitors function as tiny batteries. They are polarized. The polarity is also marked on the component housing.

Insert 10uF capacitor all the way.

Connect:


+ to pin 1

- to pin 8!

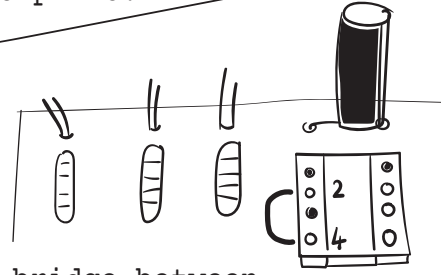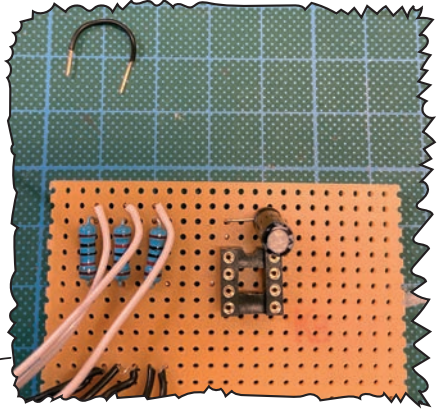


Make a bridge between pin 2 and 4 and connect them to ground.

Masse

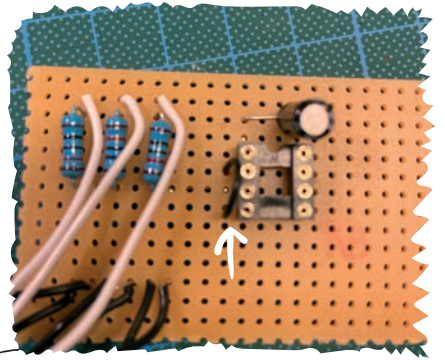

# BATTERIE CLIP TILT SWITCH


ON ↔ OFF

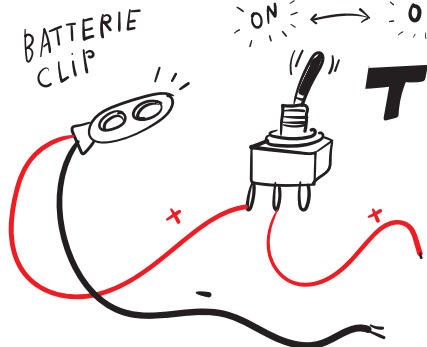


A tilt switch has on and off function.

Solder battery clip and tilt switch together.


Connect + to pin 6 and - to ground.

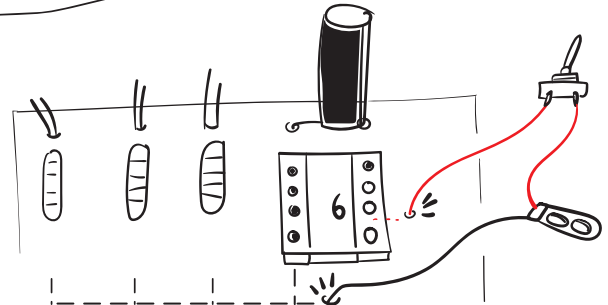


# LAUTSPRECHER

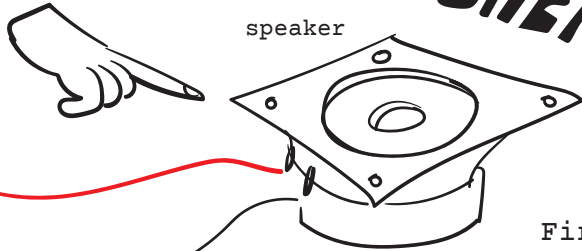

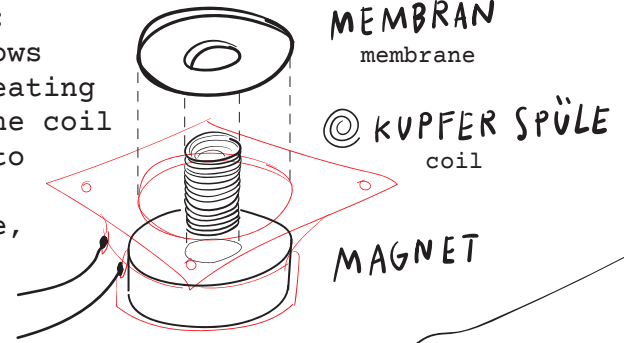
How a speaker works:  
 electric current flows  
 through the coil creating  
 a magnetic field, the coil  
 moves the membrane to  
 create sound waves.  
 A mic works the same,  
 but backwards!





First solder leads to  
 the speaker.

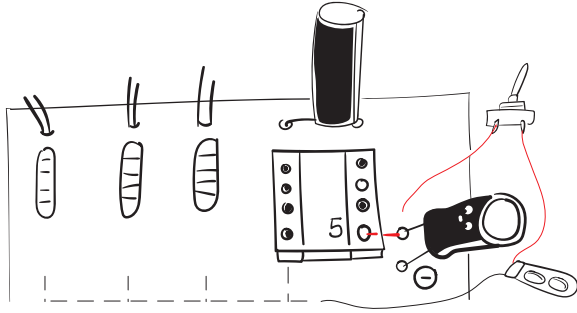

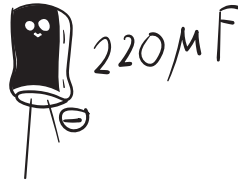
Connect 220µF capacitor:  
 + to pin 5  
 - will connect with  
 speaker.



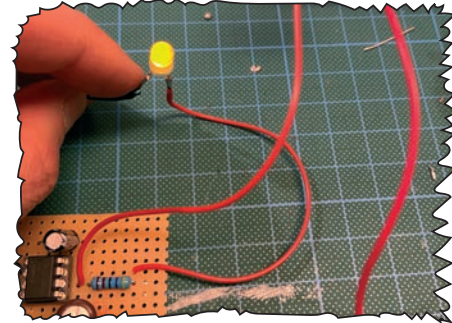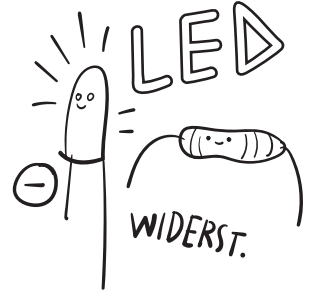
You can also  
 add an LED, to  
 show when  
 circuit is on.  
 The LED is  
 polarized, and  
 always needs a  
 resistor.



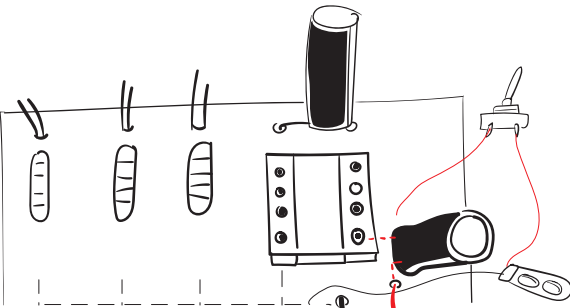Connect speaker:  
 + with capacitor  
 - with ground.




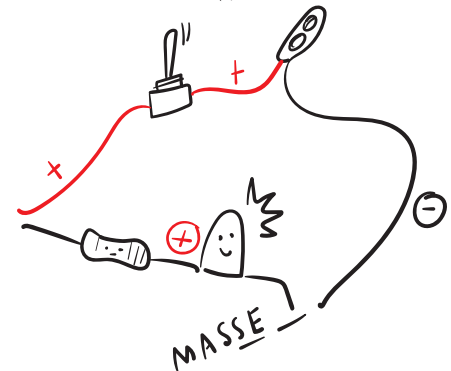Connect as  
 the diagram  
 shows, to  
 tilt switch  
 and to  
 ground.



# Mikto

microphone

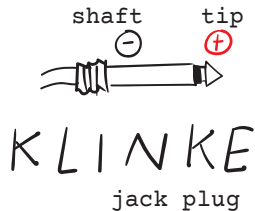


Use a mono jack plug. This is a connector for audio signal.

Follow the drawing to connect leads correctly according to polarity.

PIEZO

A piezo is a contact mic, it has a brass and a ceramic plate. It picks up vibration, and usually not our voice...

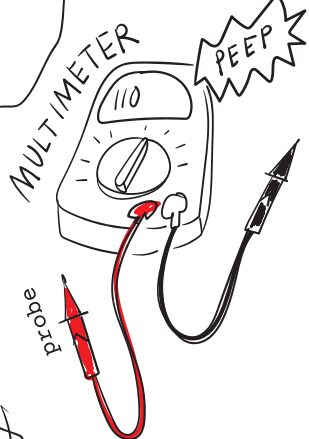Unless you put the mic inside a cone! For example the Overlock thread cone!





How to find out polarity?






Use the multimeter! Plug jack into socket. To find + touch one probe to jack tip, the other to socket terminals: If it beeps its +!

To find - touch jack shaft and socket terminals: If it beeps its -!

# SOUND CHECK

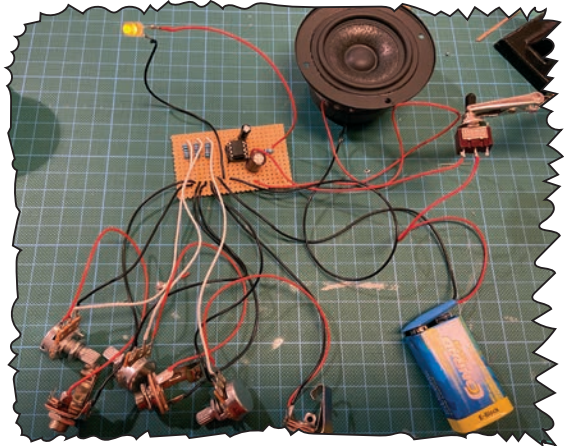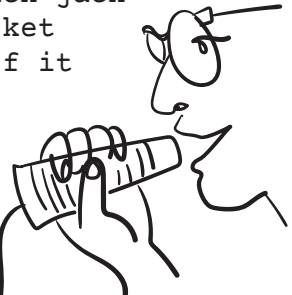

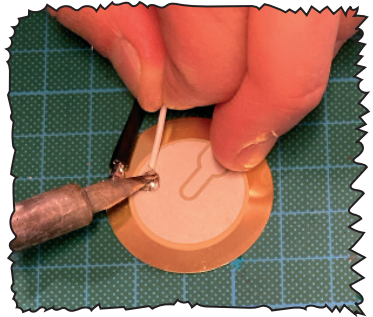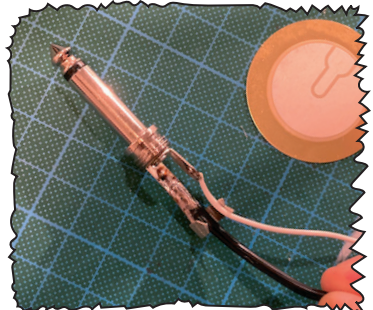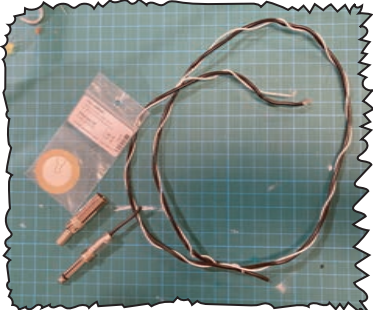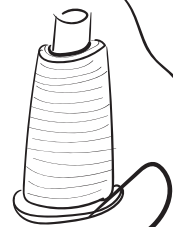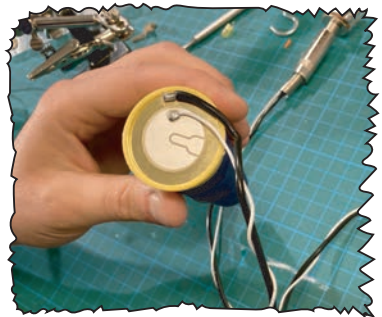Place chip, check if its the right way! Plug mic. Connect 9v battery. Tilt switch on!!!



# CASE




A case is good protection for your device! Look for cigar boxes, Plastic containers, a bag... anything that isn't metal works.

Measure to make sure everything fits in the case: leave room between the poties and jack sockets, they cannot touch each other! Shorten any leads if they are too long.

Hot glue the tilt switch onto the circuit board to secure it once the switch is placed in the case.

Mark the holes for poties, sockets, switch and LED and make holes with screwdriver.

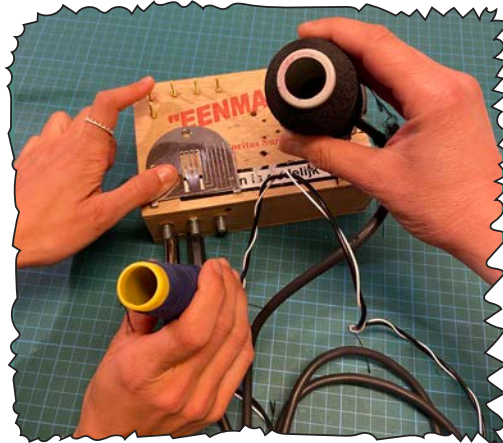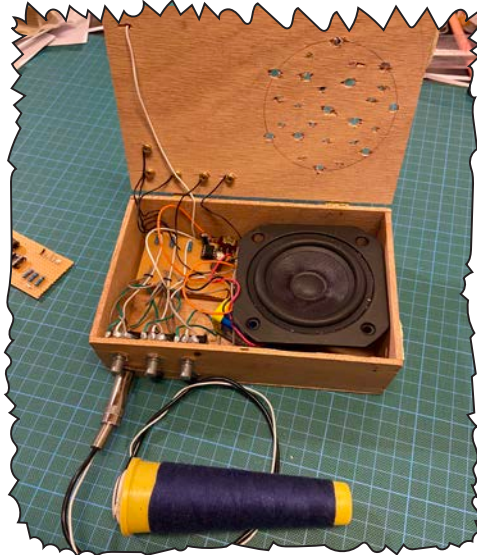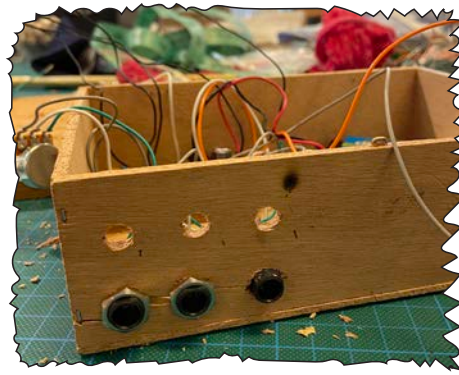
Unscrew the nuts on poties and jacks, place them inside the case and screw them tight from the outside!



TURNING YOUR MULTI-MEGA-PHONE INTO A NOISE BOX:

Touch the back of your circuit board with two fingers: at certain connections you hear some squeaks and noises. This is because our bodies conduct electricity, and actually you are making a short circuit on the board with fun results!

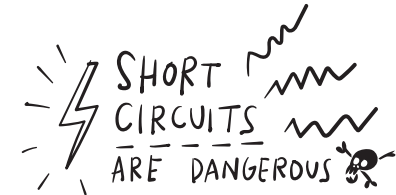Extend these points with some shielded wire to anything conductive: screws, metals... to check conductivity use the multimeter: if it beeps its conductive!



Working with short circuits as noise generators is a fun experiment but should only be played with battery operated devices!



MAKE NOISE with your friends!!!